

CCCN212 : Digital logic design



Assignment#2 CLO2.1

Student NameBeem.Abdullah Alkthyri.....

Student_ID2115561.....

Question 1: Flip Flop

Consider the following flip flop

  

1. Give the name of each flip flops used in the fig1 and fig2

1-The first one is D flip flop

2-j-k flip flop


2. Give the timing diagram for each circuit considering the signal CLK



Q15+ The truth table of the D flip flop:


| CLK | D | Q |
|-----|---|------------|
| 1 | 0 | 0 |
| 1 | 1 | 1 |
| 0 | 0 | not change |
| 0 | 1 | not change |

So in the case $D = \overline{Q}$ and in the fig 2 we know that $j=k=VCC = 1$
So the timing diagram is

 

 Question2: BCD adder

Consider a 4 bit Adder given the following figure, where A and B are 4 bit numbers:



- 1- Dress the corresponding truth table
- 2- To realize a BCD adder, we need to:
 - Step1: First add the two binary numbers A and B
 - Step2: If the sum is less or equal than 9, then the value of BCD sum and binary sum will be the same otherwise we will add 6 (0110 in binary)
- a) Dress the truth table for the BCD sum (from decimal numbers 0 to 15)
- b) Give the conditions from the truth table where we need to add 6 to the binary sum? Give a logic equation
- c) Design a BCD adder using two 4 bits' adder and gate AND and OR

1)

| A | B | Cin | Sum | Carry |
|---|---|-----|-----|-------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 12ea |

Q2)

a)

To make a truth table for BCD sum ,we need to consider the decimal number from 0 to 15 and determine their corresponding BCD sum .the BCD sum is a 4-bit number ,so we will have four output columns for the BCD sum bits (S3,S2,S1,S0)